

An aerial photograph of a large, multi-story university building with a central tower and a brown tiled roof. In front of the building is a large, circular green lawn with a central circular garden bed. The lawn is surrounded by palm trees and a paved road with several cars. The background shows a cityscape and distant hills under a clear sky.

# BASIC ELECTRONIC CIRCUITS


**Tutorial: Amplifier and OP-amp**

1. Consider the voltage amplifier circuit model,  $A_{vo} = 100 \text{ V/V}$ , under the following conditions; calculate the overall gain in each case and express in dB.

(a)  $R_i = 10R_s, R_L = 10R_o$


(b)  $R_i = R_s, R_L = R_o$

(c)  $R_i = R_s/10, R_L = R_o/10$

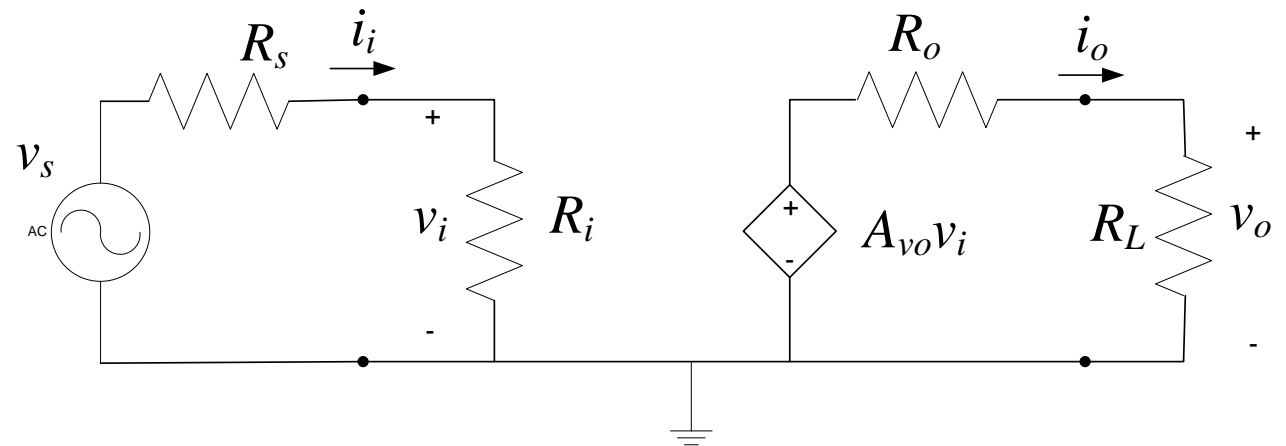


2. You are given two amplifiers, A and B, to connect in cascade between a 10-mV, 100 k $\Omega$  source and a 100  $\Omega$  load. The amplifiers have voltage gain, input resistance, and output resistance as follows: for A, 100 V/V, 100 k $\Omega$ , 10 k $\Omega$ , respectively; for B, 10 V/V, 10 k $\Omega$ , 1 k $\Omega$ , respectively. Your problem is to decide how the amplifiers should be connected. To proceed, evaluate the two possible connections between source S and load L, namely, SABL and SBAL. Find the voltage gain for each both as a ratio and in decibels. Which amplifier arrangement is best?


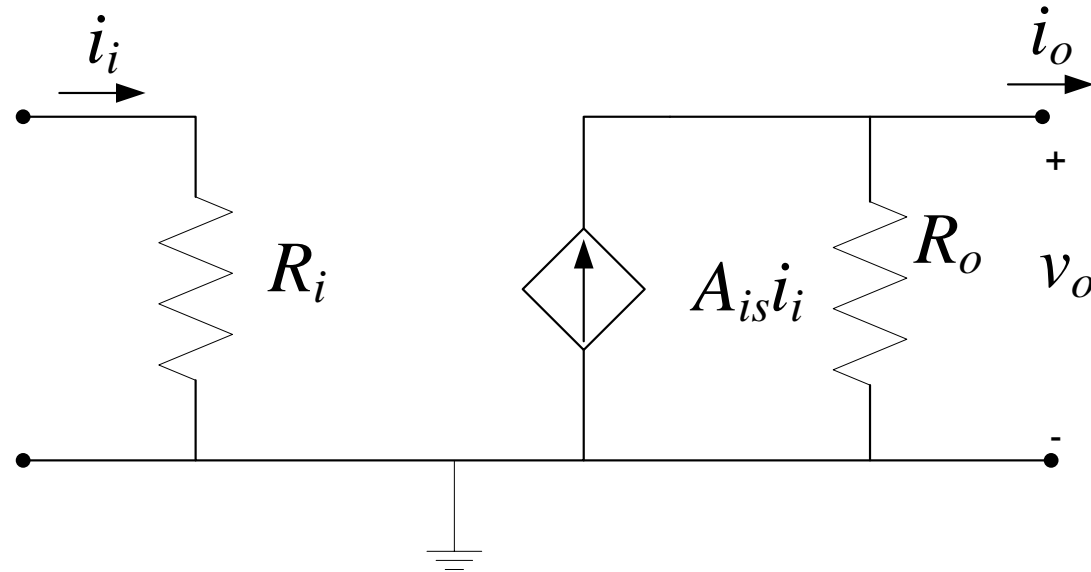
3. A current amplifier for which  $R_i = 100\ \Omega$ ,  $R_o = 10\ \text{k}\Omega$ , and  $A_{is} = 100\ \text{A/A}$  is to be connected between a 100 mV source with a resistance of  $10\ \text{k}\Omega$  and a load of  $1\ \text{k}\Omega$ . What are the values of current gain  $i_o/i_i$ , of voltage gain  $v_o/v_s$ , and of power gain expressed directly and in decibels?



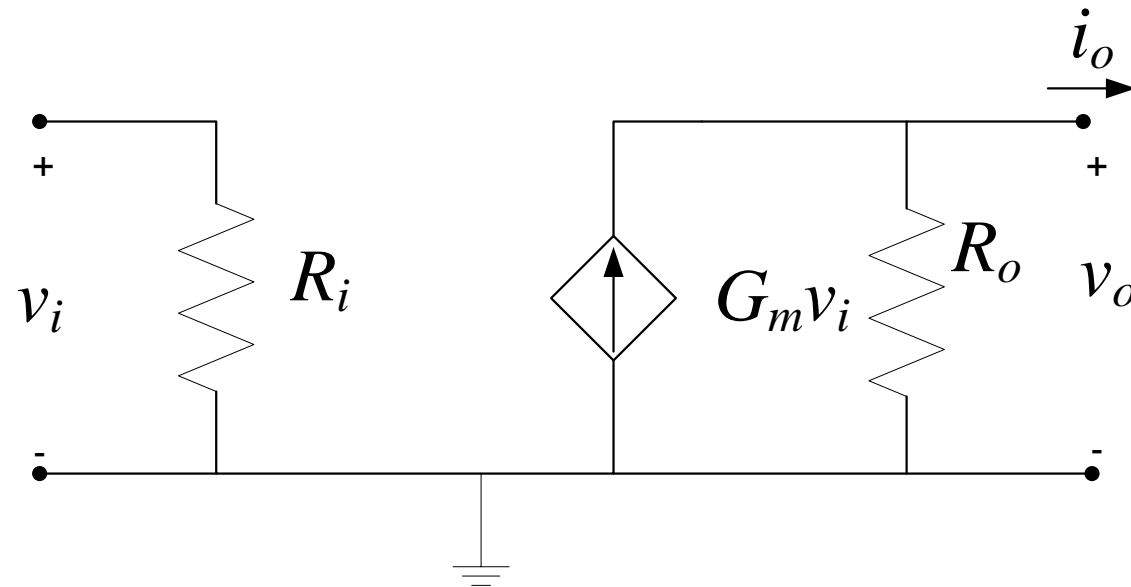4. A transconductance amplifier with  $R_i = 2 \text{ k } \Omega$ ,  $G_m = 60 \text{ mA/V}$ , and  $R_o = 20 \text{ k } \Omega$  is fed with a voltage source having a source resistance of  $1 \text{ k } \Omega$  and is loaded with a  $1 \text{ k } \Omega$  resistance. Find the voltage gain realized.



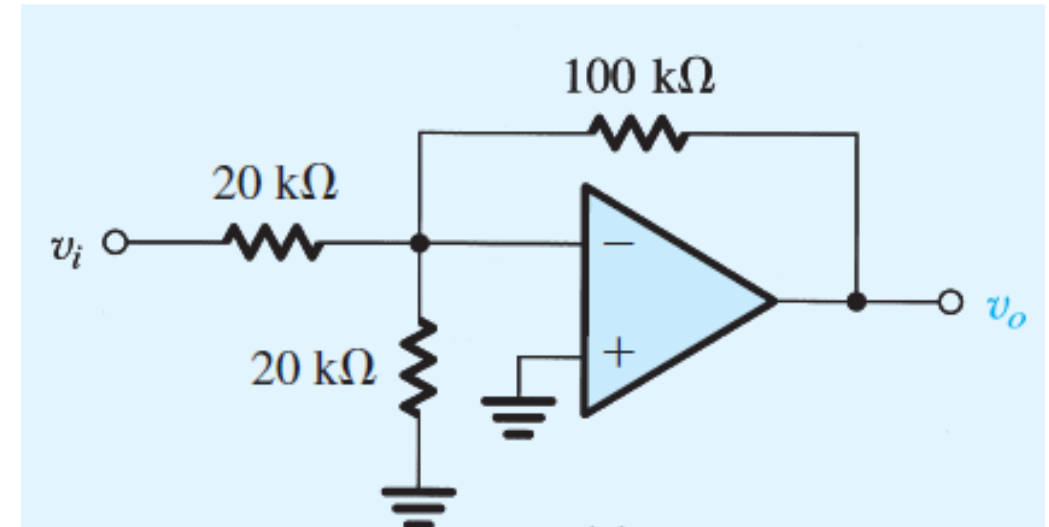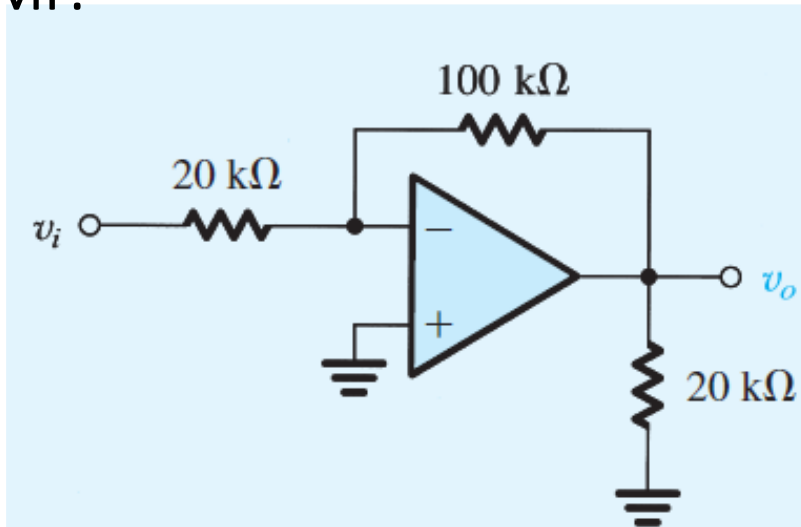5. Calculate current through each resistor, voltage at each terminal of the OP-AMP.




6. For the non-inverting configuration, determine the closed-loop gain of the op-amp circuits with following resistive networks, also determine the current through each resistor and voltage at each terminal of the op-amp.


(i)  $R_1 = 10\text{ k}\Omega$ ;  $R_f = 100\text{ k}\Omega$ .

(ii)  $R_1 = 1\text{ k}\Omega$ ;  $R_f = 1\text{ M}\Omega$ ;  $R_L = 5\text{ k}\Omega$ .

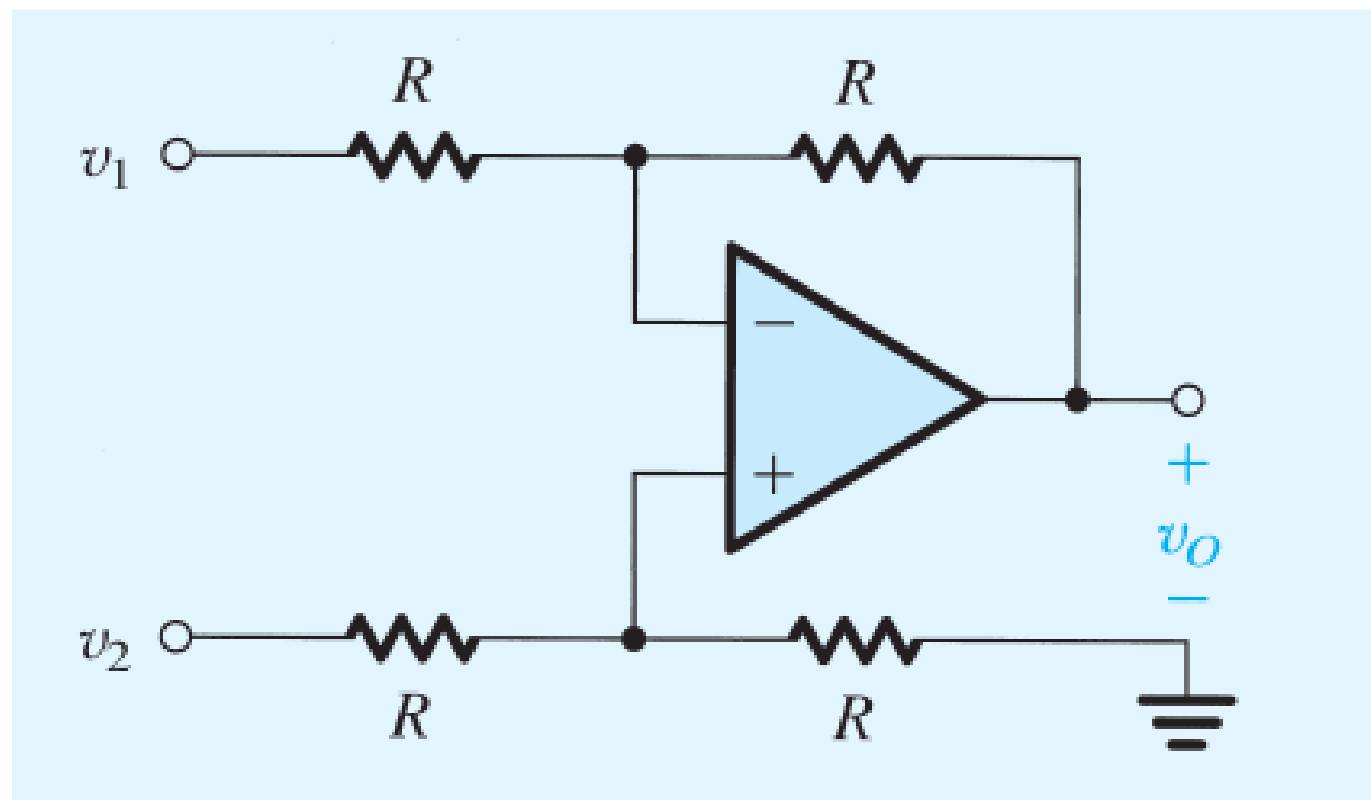7. Express  $v_o$  in terms of  $v_1$  and  $v_2$ .



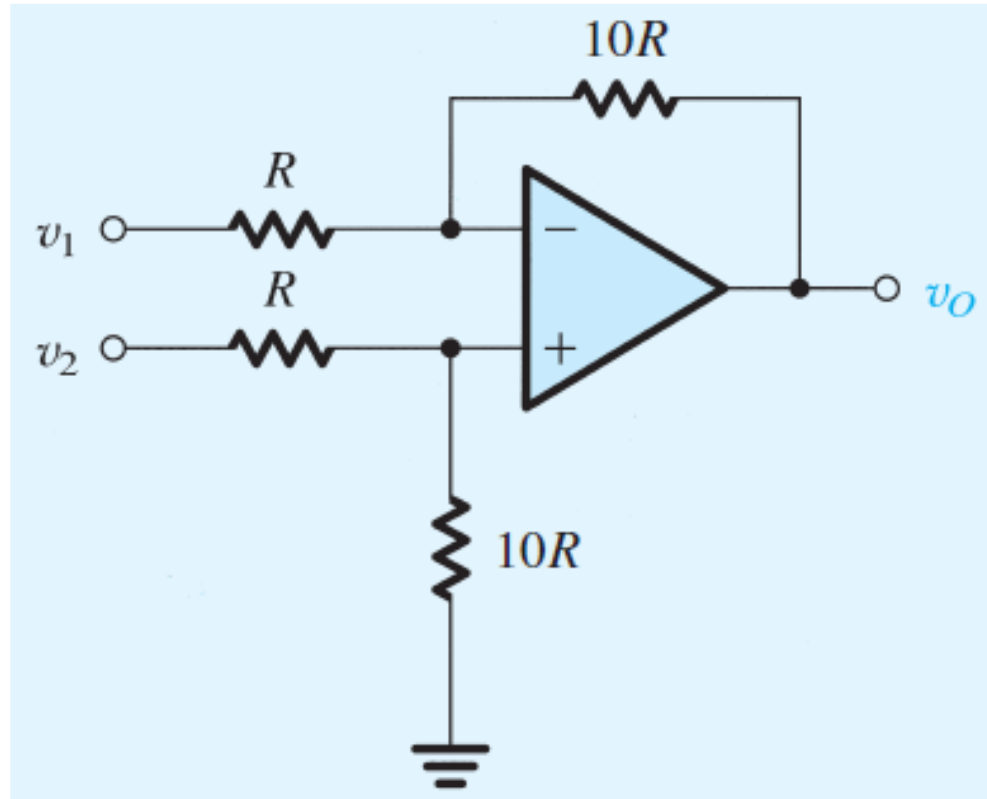8. Use superposition to determine  $v_o$  in terms of  $v_1$  and  $v_2$ .



$$v_1 = 10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 1000t), \text{ volts}$$

$$v_2 = 10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 1000t), \text{ volts}$$