

An aerial photograph of a large, multi-story university building with a central tower and a brown roof. In front of the building is a large green lawn with a circular garden bed in the center. The lawn is surrounded by palm trees and a paved road with some cars. The background shows a cityscape and hills under a clear sky.

BASIC ELECTRONIC CIRCUITS

Two-port Network Parameters

Content

- One-port network and two-port network
- Admittance Parameters
- Impedance Parameters
- Hybrid Parameters
- Transmission Parameters

One-port Network

- A terminal is a **connecting wire** thorough which **the electrical energy or signal** that **enter** (**input terminal**) into a network or **leave** (**output terminal**) the network.
- A pair of terminals at which a signal may enter or leave network is called a "**PORT**".
- A network having only one such pair is called one-port network.
- More than one pair of terminals is present, "Multiport network".

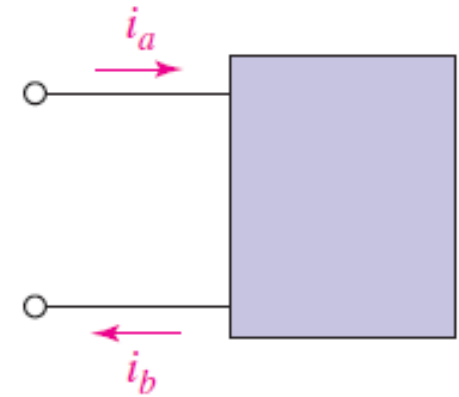


Fig. 1. One-port network.

Two-port Network

- Describes the relation between the input and output terminals.
- Linear networks
- No independent source should present in the network.
- Dependent source may present.


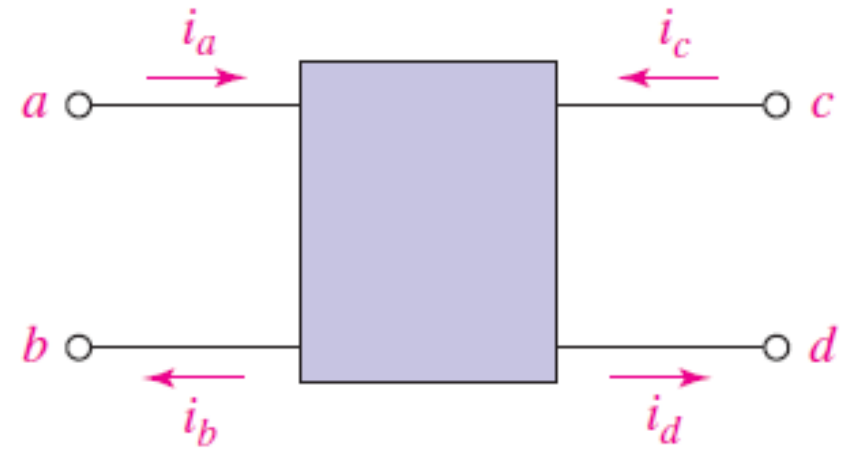


Fig. 2. Two-port network.

Admittance (Y) Parameters

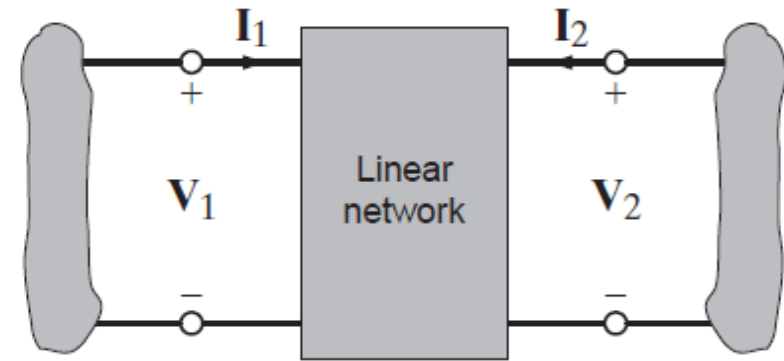- Linear network with No independent sources.
- V_1 and V_2 are applied voltage and I_1 and I_2 are the responses.



- BY using the superposition:

- $I_1 = Y_{11}V_1 + Y_{12}V_2$
- $I_2 = Y_{21}V_1 + Y_{22}V_2$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Y-parameters: Short circuit admittance parameters

- Short-Circuit input admittance - Y_{11}
- Short circuit transfer admittances - Y_{12}, Y_{21}
- Short-circuit output admittance - Y_{22} .
- Properties: Reciprocal ($Y_{12} = Y_{21}$); Symmetric ($Y_{11} = Y_{22}$)

$$\begin{aligned} y_{11} &= \frac{I_1}{V_1} \bigg|_{V_2=0} \\ y_{12} &= \frac{I_1}{V_2} \bigg|_{V_1=0} \\ y_{21} &= \frac{I_2}{V_1} \bigg|_{V_2=0} \\ y_{22} &= \frac{I_2}{V_2} \bigg|_{V_1=0} \end{aligned}$$

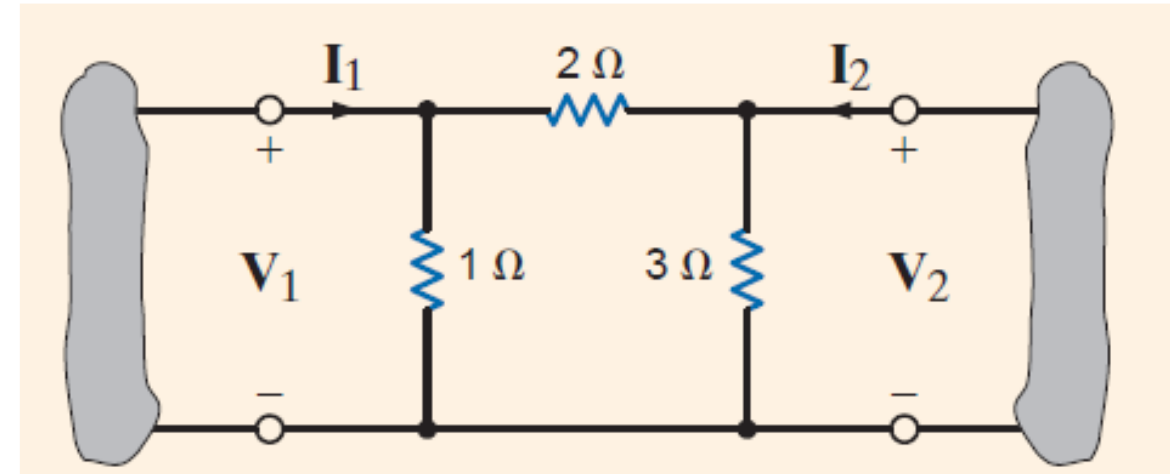- Ex: Determine the Y parameters of the network.
- Further, determine the current in a $4\ \Omega$ load, which is connected to the output port when a 2 A current source is applied at the input port.



$$I_1 = \frac{3}{2}V_1 - \frac{1}{2}V_2 \quad I_2 = -\frac{1}{2}V_1 + \frac{5}{6}V_2$$


$$I_1 = 2\text{ A} \quad \text{and} \quad V_2 = -4I_2$$

$$2 = \frac{3}{2}V_1 - \frac{1}{2}V_2$$


$$0 = -\frac{1}{2}V_1 + \frac{13}{12}V_2$$

$$V_2 = 8/11\text{ V} \quad \text{and therefore} \quad I_2 = -2/11\text{ A.}$$

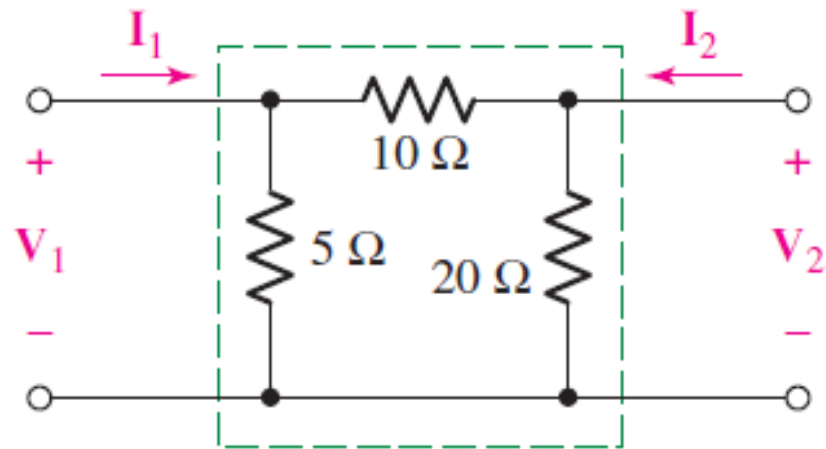- Determine the Y-parameters of the following networks.



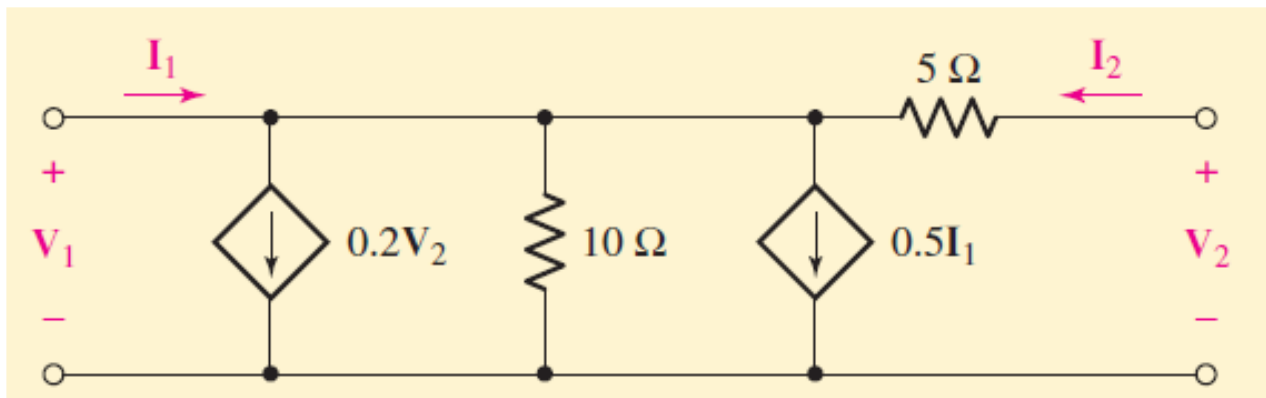
$$y = \begin{bmatrix} 0.3 & -0.1 \\ -0.1 & 0.15 \end{bmatrix}$$



$$\begin{bmatrix} 0.6 & 0 \\ -0.2 & 0.2 \end{bmatrix}$$

Impedance (Z) parameters: Open-circuit impedance parameters

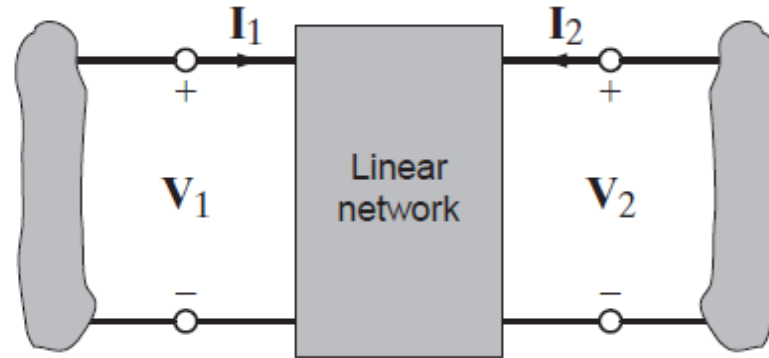- $V_1 = Z_{11}I_1 + Z_{12}I_2$
- $V_2 = Z_{21}I_1 + Z_{22}I_2$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- Open-Circuit input impedance - Z_{11}
- Open circuit transfer impedances - Z_{12}, Z_{21}
- Open-circuit output impedance - Z_{22} .


$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

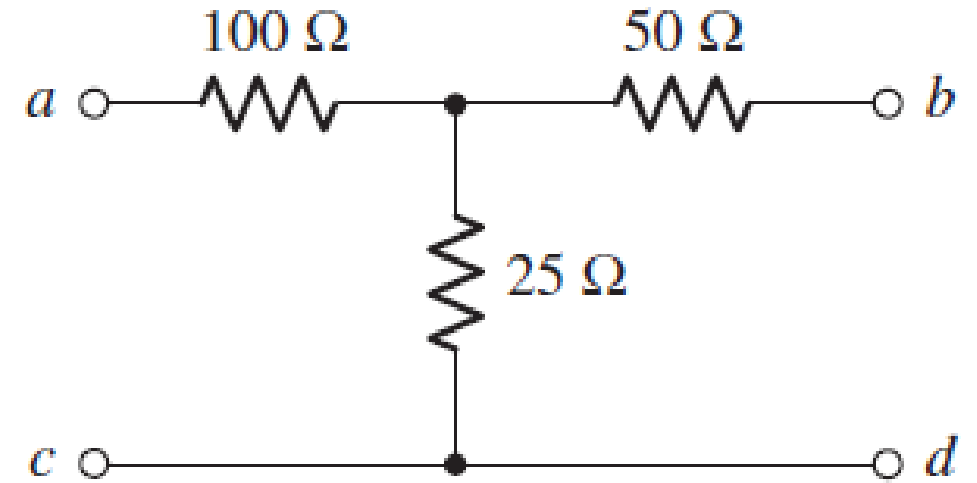
- Ex: Determine the Z parameters of the network.
- Further, determine the currents, when a $25\ \Omega$ load is connected to the output port when a 5 V voltage source is applied at the input port.




$$Z_{11} = 125\ \Omega; Z_{12} = 25\ \Omega; Z_{21} = 25\ \Omega; Z_{22} = 75\ \Omega.$$

$$I_2 = -1\text{ mA}; V_2 = 0.26\text{ V}; I_1 = 42\text{ mA}$$

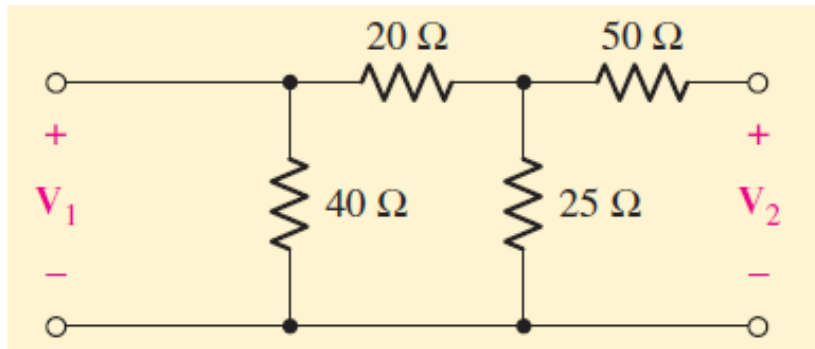- Ex: Determine the Impedance parameters:


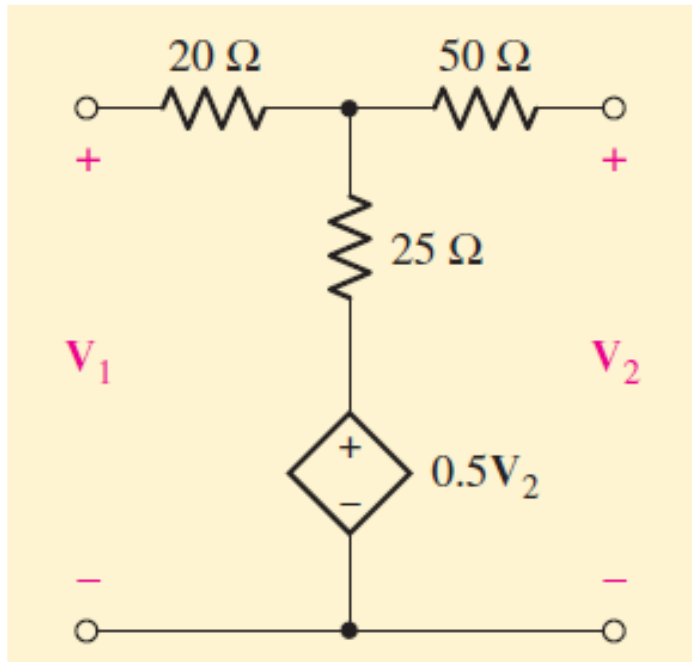
$$\begin{bmatrix} 21.2 & 11.76 \\ 11.76 & 67.6 \end{bmatrix} (\Omega)$$



$$\begin{bmatrix} 70 & 100 \\ 50 & 150 \end{bmatrix} (\Omega)$$

Hybrid (h) Parameters

- Difficulties in measuring the transfer parameters (Z_{21}).

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \text{short-circuit input impedance}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \text{short-circuit forward current gain}$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$



$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \text{open-circuit reverse voltage gain}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \text{open-circuit output admittance}$$

- Ex: Determine the hybrid parameters of the bilateral resistive network

$$\begin{bmatrix} 3.4 \, \Omega & 0.4 \\ -0.4 & 0.1 \, \text{S} \end{bmatrix}$$
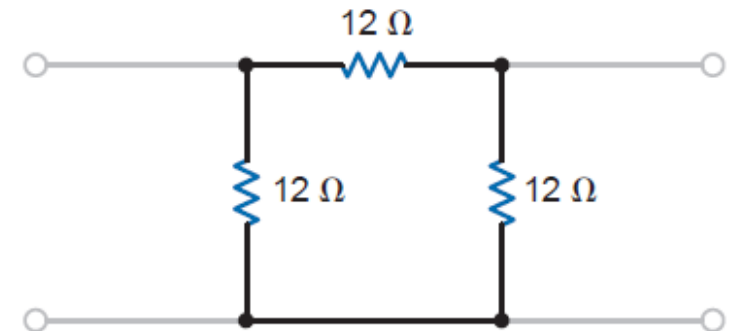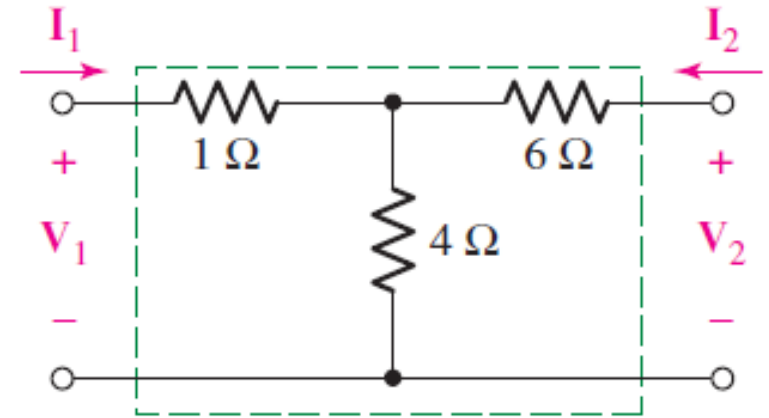
$$h_{11} = 6 \, \Omega; h_{12} = 0.5; h_{21} = -0.5; h_{22} = 0.125 \, \text{S}.$$



Transmission (t) or (ABCD) parameters

$$\mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2$$

$$\mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2$$

- A - Open circuit reverse voltage gain
- B - Short circuit transfer impedance
- C - Open circuit transfer admittance
- D - Short circuit reverse current gain

$$\mathbf{A} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0}$$


$$\mathbf{B} = \left. \frac{\mathbf{V}_1}{-\mathbf{I}_2} \right|_{\mathbf{V}_2=0}$$

$$\mathbf{C} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0}$$

$$\mathbf{D} = \left. \frac{\mathbf{I}_1}{-\mathbf{I}_2} \right|_{\mathbf{V}_2=0}$$


- Obtain the Transmission parameters
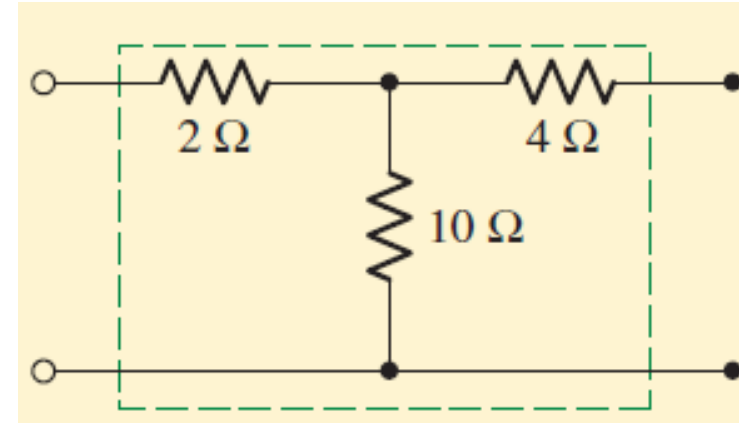
$$\mathbf{t}_A = \begin{bmatrix} 1.2 & 6.8 \, \Omega \\ 0.1 \, \text{S} & 1.4 \end{bmatrix}$$



Two-port parameters of a series and shunt elements

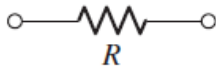Y-parameters Z-parameters h-parameters ABCD Parameters




$$\begin{bmatrix} 1/R & -1/R \\ -1/R & 1/R \end{bmatrix}$$

$$\begin{bmatrix} \infty & \infty \\ \infty & \infty \end{bmatrix}$$

$$\begin{bmatrix} R & 1 \\ -1 & 0 \end{bmatrix}$$
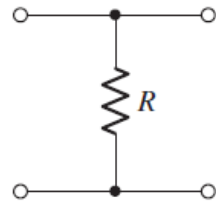
$$\begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$



$$\begin{bmatrix} \infty & \infty \\ \infty & \infty \end{bmatrix}$$


$$\begin{bmatrix} R & R \\ R & R \end{bmatrix}$$

$$\begin{bmatrix} 0 & 1 \\ -1 & 1/R \end{bmatrix}$$


$$\begin{bmatrix} 1 & 0 \\ 1/R & 1 \end{bmatrix}$$

Types of Interconnection of two-ports


- Parallel connection:

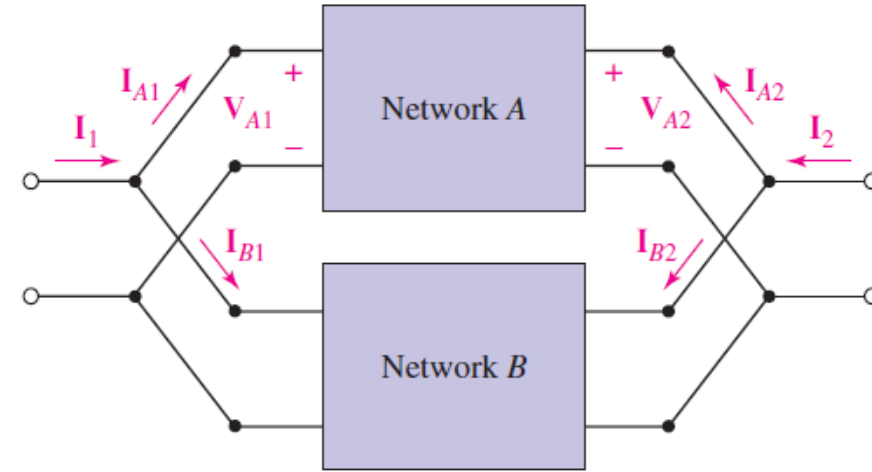

- Series Connection:

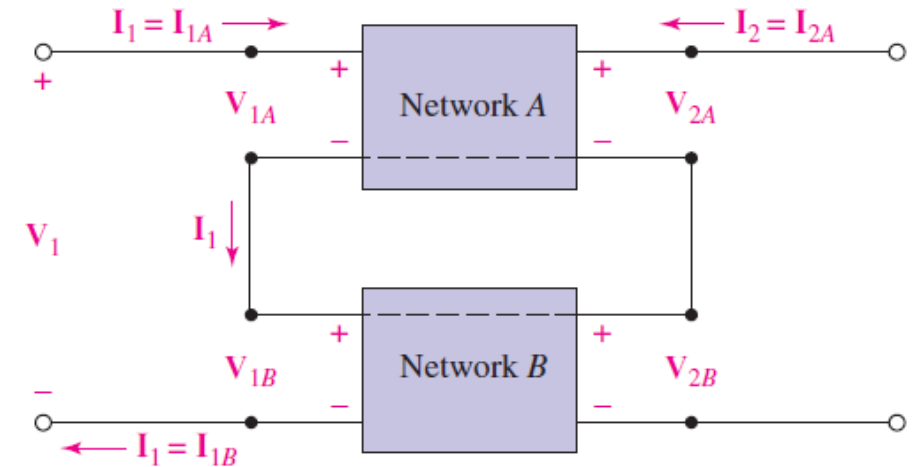

- Cascade Connection:

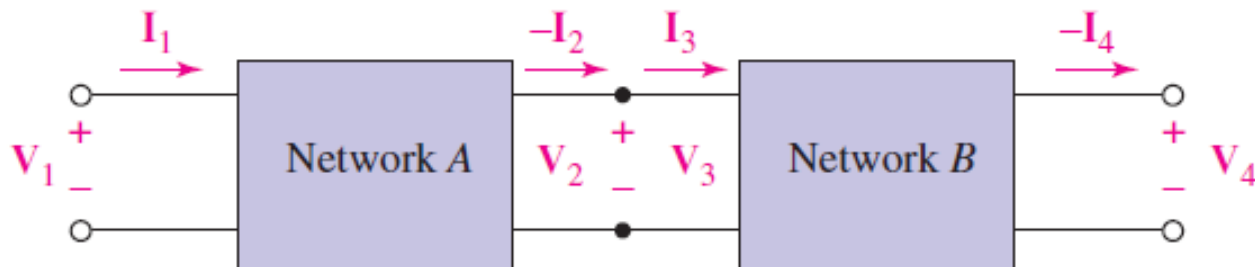

Analysis of Parallel Connection:

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

- For parallel connection:

$$I_1 = I_{A1} + I_{B1}$$

$$V_1 = V_{A1} = V_{B1}$$

$$I_2 = I_{A2} + I_{B2}$$

$$V_2 = V_{A2} = V_{B2}$$

- Y parameters of network A:

$$I_{A1} = Y_{11A}V_{A1} + Y_{12A}V_{A2} \quad I_{A2} = Y_{21A}V_{A1} + Y_{22A}V_{A2}$$


- Y parameters of Network B:

$$I_{B1} = Y_{11B}V_{B1} + Y_{12B}V_{B2} \quad I_{B2} = Y_{21B}V_{B1} + Y_{22B}V_{B2}$$

- Finally,

$$I_1 = (Y_{11A} + Y_{11B})V_1 + (Y_{12A} + Y_{12B})V_2$$
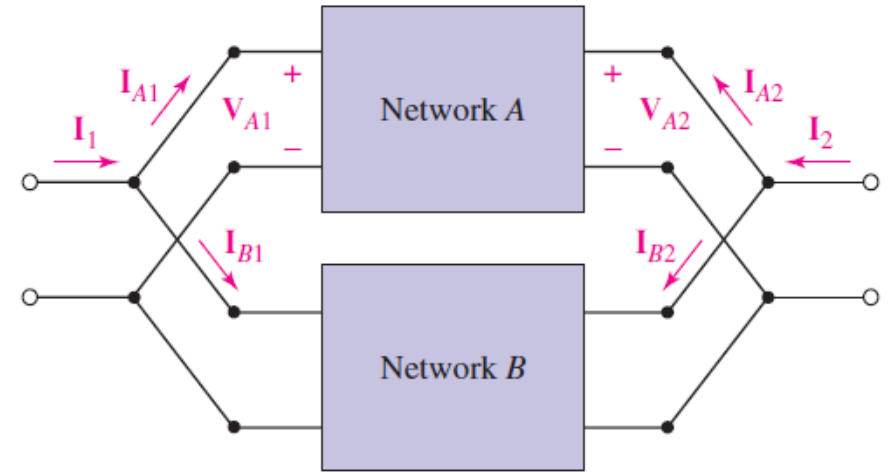
$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_{11A} + Y_{11B} & Y_{12A} + Y_{12B} \\ Y_{21A} + Y_{21B} & Y_{22A} + Y_{22B} \end{bmatrix}$$



Analysis of Series Connection:

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

- For series connection:

$$V_1 = V_{1A} + V_{1B}$$

$$I_1 = I_{1A} = I_{1B}$$

$$V_2 = V_{2A} + V_{2B}$$

$$I_2 = I_{2A} = I_{2B}$$

- Z parameters of network A:

$$V_{1A} = Z_{11A}I_{1A} + Z_{12A}I_{2A} \quad V_{2A} = Z_{21A}I_{1A} + Z_{22A}I_{2A}$$


- Z parameters of Network B:

$$V_{1B} = Z_{11B}I_{1B} + Z_{12B}I_{2B} \quad V_{2B} = Z_{21B}I_{1B} + Z_{22B}I_{2B}$$

- Finally,

$$V_1 = (Z_{11A} + Z_{11B})I_1 + (Z_{12A} + Z_{12B})I_2$$
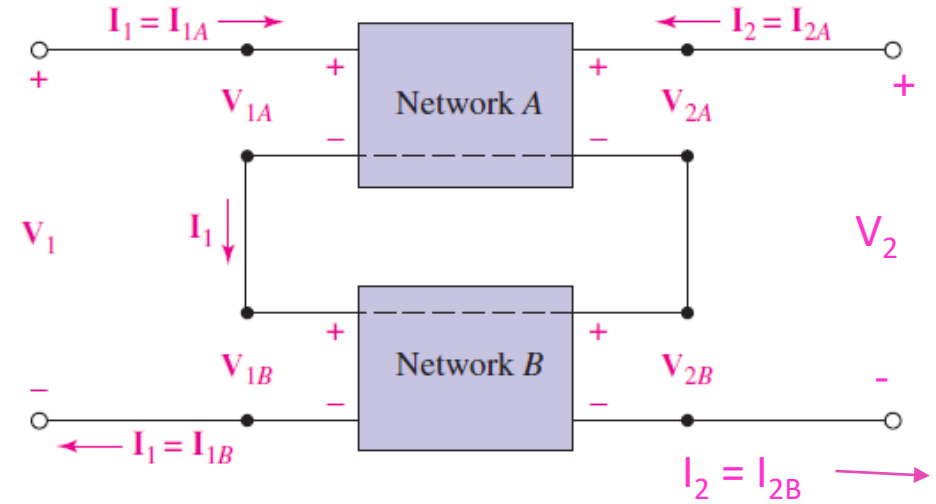
$$V_2 = (Z_{21A} + Z_{21B})I_1 + (Z_{22A} + Z_{22B})I_2$$



$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11A} + Z_{11B} & Z_{12A} + Z_{12B} \\ Z_{21A} + Z_{21B} & Z_{22A} + Z_{22B} \end{bmatrix}$$

Analysis of Cascade Connection:

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

- For a cascade connection:

$$V_2 = V_3$$

$$-I_2 = I_3$$


- ABCD parameters of network A:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_A & B_A \\ C_A & D_A \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

- ABCD parameters of Network B:

$$\begin{bmatrix} V_3 \\ I_3 \end{bmatrix} = \begin{bmatrix} A_B & B_B \\ C_B & D_B \end{bmatrix} \begin{bmatrix} V_4 \\ -I_4 \end{bmatrix}$$


- Finally,

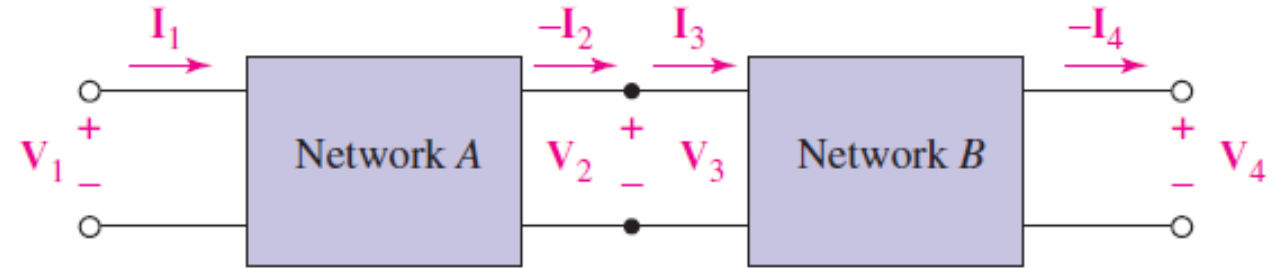

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_A & B_A \\ C_A & D_A \end{bmatrix} \begin{bmatrix} A_B & B_B \\ C_B & D_B \end{bmatrix} \begin{bmatrix} V_4 \\ -I_4 \end{bmatrix}$$

Parameter conversions

- Z parameters to ABCD parameters

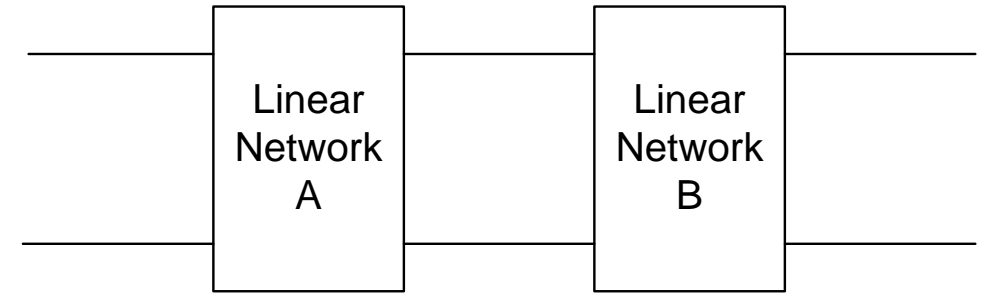

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow \textcircled{1}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow \textcircled{2}$$

Rewriting eq. 2,

$$I_1 = \frac{1}{Z_{21}}V_2 - \frac{Z_{22}}{Z_{21}}I_2 \rightarrow \textcircled{5}$$

Using I_1 in eq. 1,

$$V_1 = \frac{Z_{11}}{Z_{21}}V_2 - \frac{\Delta Z}{Z_{21}}I_2 \rightarrow \textcircled{6}$$

$$\Delta Z = Z_{11}Z_{22} - Z_{21}Z_{12}$$

$$V_1 = AV_2 - BI_2 \rightarrow \textcircled{3}$$

$$I_1 = CV_2 - DI_2 \rightarrow \textcircled{4}$$

By comparing eq. 6 with eq. 3 and eq. 5 with eq. 4,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta Z}{Z_{21}} \\ 1 & \frac{Z_{22}}{Z_{21}} \end{bmatrix}$$

- Z parameters to h parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow \textcircled{1}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow \textcircled{2}$$

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow \textcircled{3}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow \textcircled{4}$$

Rewriting eq. 2,

$$I_2 = -\frac{Z_{21}}{Z_{22}}I_1 + \frac{1}{Z_{22}}V_2 \rightarrow \textcircled{5}$$

By comparing eq. 6 with eq. 3 and eq. 5 with eq. 4,

Using I_2 in eq. 1,

$$V_1 = \frac{\Delta Z}{Z_{22}}I_1 + \frac{Z_{12}}{Z_{22}}V_2 \rightarrow \textcircled{6}$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{\Delta Z}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ -\frac{Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix}$$

$$\Delta Z = Z_{11}Z_{22} - Z_{21}Z_{12}$$

- Z parameters to Y parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow \textcircled{1}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow \textcircled{2}$$

In Matrix form,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Multiplication with inverse matrix of Z,

$$[Z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [Z]^{-1} [Z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[Z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [Z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \rightarrow \textcircled{5}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \rightarrow \textcircled{3}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \rightarrow \textcircled{4}$$

In Matrix form,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \rightarrow \textcircled{6}$$

From 5 and 6

$$[Y] = [Z]^{-1}$$

Finally,

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \frac{1}{\Delta Z} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$

$$\Delta Z = Z_{11}Z_{22} - Z_{21}Z_{12}$$

- For a two port network, the open circuit voltage at the output terminals is 3 V when a 5 V source is connected to its input terminals (3 A current is supplied by 5 V source) and the open circuit voltage at the input terminals is 5 V when a 10 V source is connected to its output terminals (6 A current is supplied by the 10 V source), determine the transmission parameters of the two-port network.

	y		z		h		t	
y	y_{11}	y_{12}	$\frac{z_{22}}{\Delta_z}$	$\frac{-z_{12}}{\Delta_z}$	$\frac{1}{h_{11}}$	$\frac{-h_{12}}{h_{11}}$	$\frac{t_{22}}{t_{12}}$	$\frac{-\Delta_t}{t_{12}}$
	y_{21}	y_{22}	$\frac{-z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$\frac{-1}{t_{12}}$	$\frac{t_{11}}{t_{12}}$
z	$\frac{y_{22}}{\Delta_y}$	$\frac{-y_{12}}{\Delta_y}$	z_{11}	z_{12}	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{t_{11}}{t_{21}}$	$\frac{\Delta_t}{t_{21}}$
	$\frac{-y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	z_{21}	z_{22}	$\frac{-h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{t_{21}}$	$\frac{t_{22}}{t_{21}}$
h	$\frac{1}{y_{11}}$	$\frac{-y_{12}}{y_{11}}$	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	h_{11}	h_{12}	$\frac{t_{12}}{t_{22}}$	$\frac{\Delta_t}{t_{22}}$
	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	$\frac{-z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	h_{21}	h_{22}	$\frac{-1}{t_{22}}$	$\frac{t_{21}}{t_{22}}$
t	$\frac{-y_{22}}{y_{21}}$	$\frac{-1}{y_{21}}$	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$\frac{-\Delta_h}{h_{21}}$	$\frac{-h_{11}}{h_{21}}$	t_{11}	t_{12}
	$\frac{-\Delta_y}{y_{21}}$	$\frac{-y_{11}}{y_{21}}$	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$\frac{-h_{22}}{h_{21}}$	$\frac{-1}{h_{21}}$	t_{21}	t_{22}

For all parameter sets: $\Delta_p = p_{11}p_{22} - p_{12}p_{21}$.