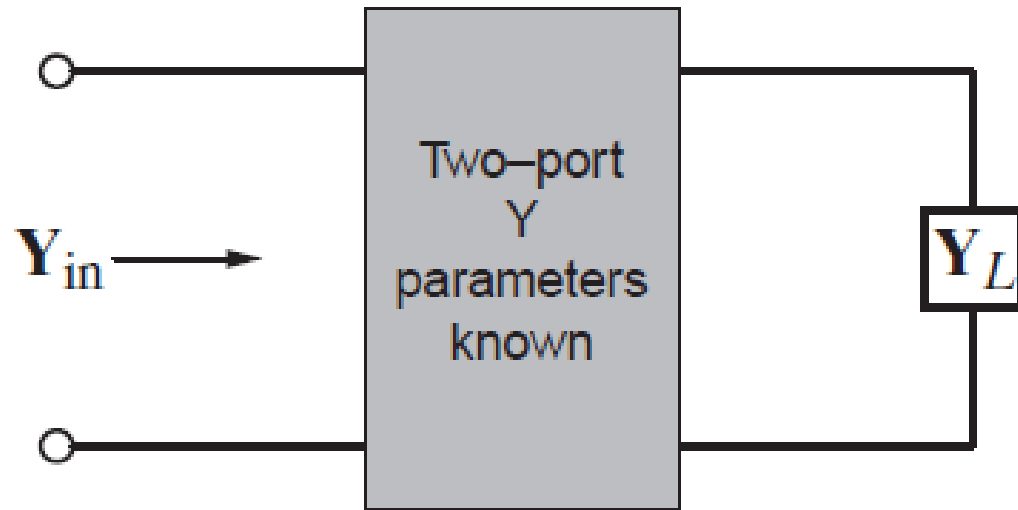




# BASIC ELECTRONIC CIRCUITS

**Tutorial: Two-port networks**  
**Feb. 8<sup>th</sup> 2019**


Find the input admittance of a two-port network, in terms of  $Y$  parameters and load  $Y_L$ .



$$\frac{I_1}{V_1} = \frac{Y_{11}Y_L + Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_L + Y_{22}}$$


Draw the circuit diagram (with all passive elements in ohms) for the network that has the following  $Y$  parameters.
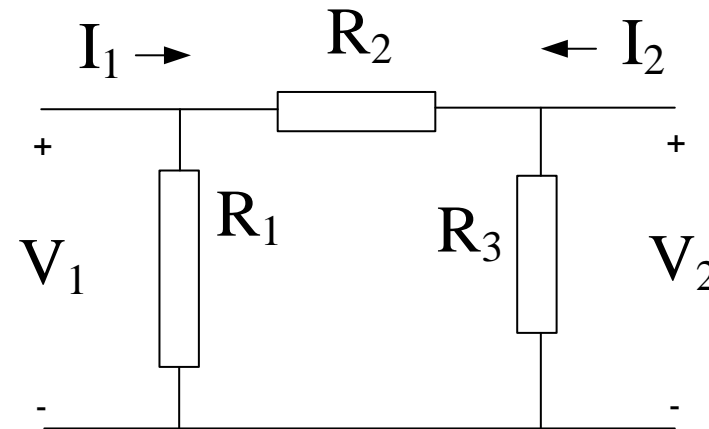
$$[Y] = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{6} \end{bmatrix}$$




$$R_1 = 1\Omega ; R_2 = 2\Omega ; R_3 = 3\Omega .$$

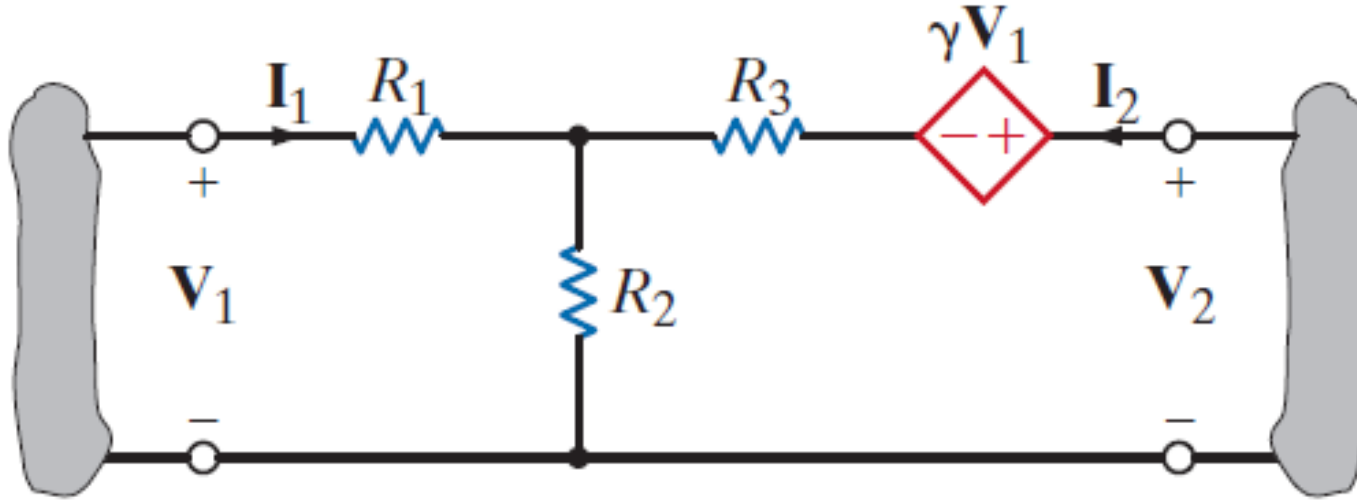Find the Z parameters of the following networks.



$$\begin{bmatrix} R_1 + R_2 & R_2 \\ \gamma(R_1 + R_2) + R_2 & R_2(\gamma + 1) + R_3 \end{bmatrix}$$

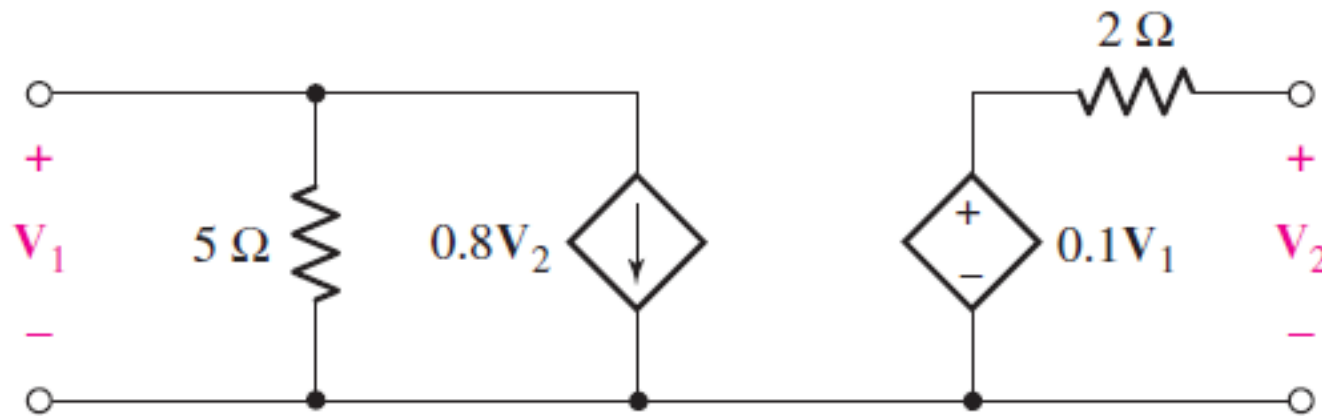Obtain the Z parameters of the network shown, and determine  $I_1$  and  $I_2$  for  $V_1 = 5 \text{ V}$  and  $V_2 = 0 \text{ V}$ .




$$\begin{bmatrix} 3.57 & -5.71 \\ 0.357 & 1.43 \end{bmatrix}$$

$$I_1 = 1 \text{ A} ; I_2 = -0.25 \text{ A}.$$


The two-port network has following hybrid parameters, Determine  $I_1$ ,  $I_2$ ,  $V_1$  and  $V_2$ .
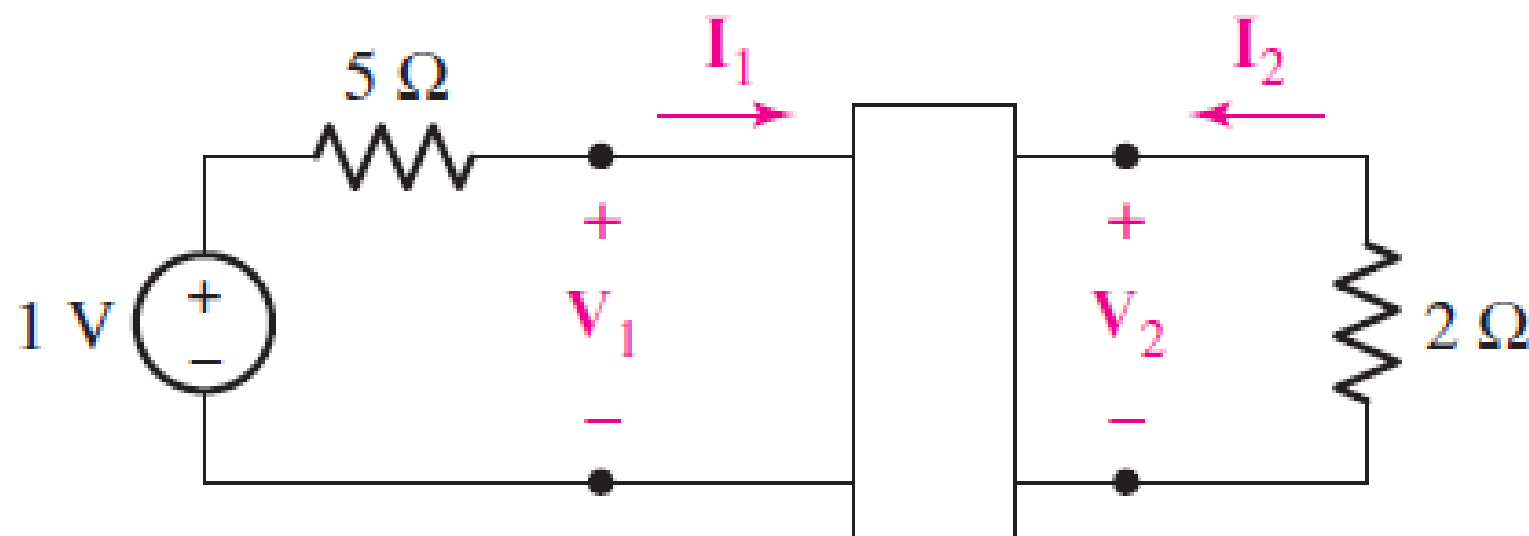
$$h = \begin{bmatrix} 1 \Omega & -1 \\ 2 & 0.5 S \end{bmatrix}$$



$$V_1 = 3/8 \text{ v}; V_2 = -1/4 \text{ v}; I_1 = I_2 = 1/8 \text{ A.}$$

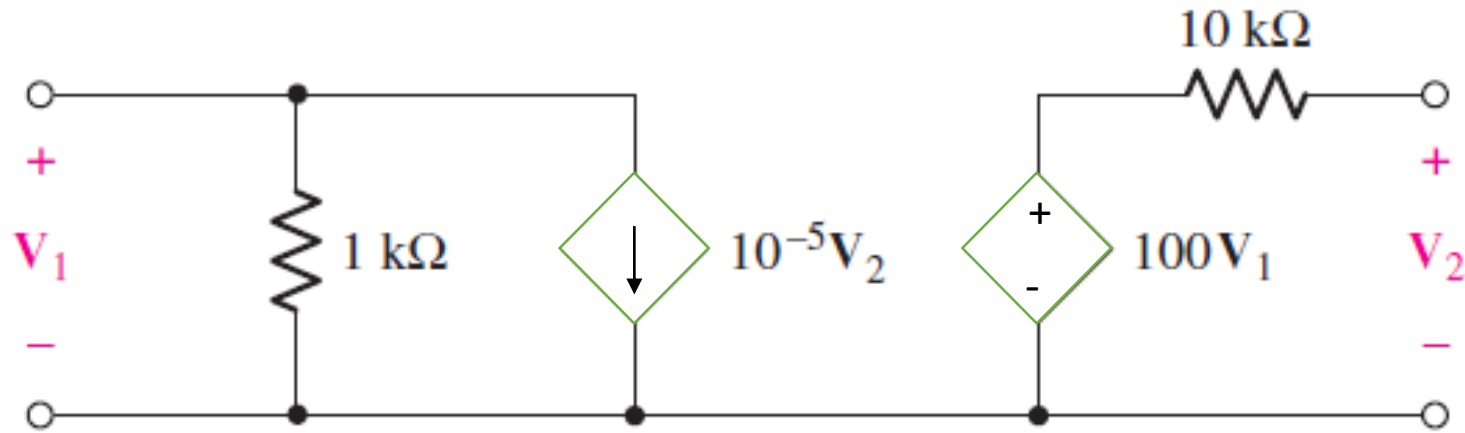Obtain the T (ABCD) parameters of the network shown, and determine  $V_2$ ,  $I_1$  and  $I_2$  when  $V_1 = 10$  V and a load of  $10\text{ k}\Omega$  is connected across the output terminals.



$$T = \begin{bmatrix} 0.01 & 100 \\ 20\ \mu S & 0.1 \end{bmatrix}$$

$$V_2 = 500\text{ v}; I_1 = 15\text{ mA}; I_2 = -0.05\text{ A}.$$