




# BASIC ELECTRONIC CIRCUITS



Tutorial

- Find  $V_o$  using the superposition

**ANSWER:**  $V_o = 5.6 \text{ V}$ .

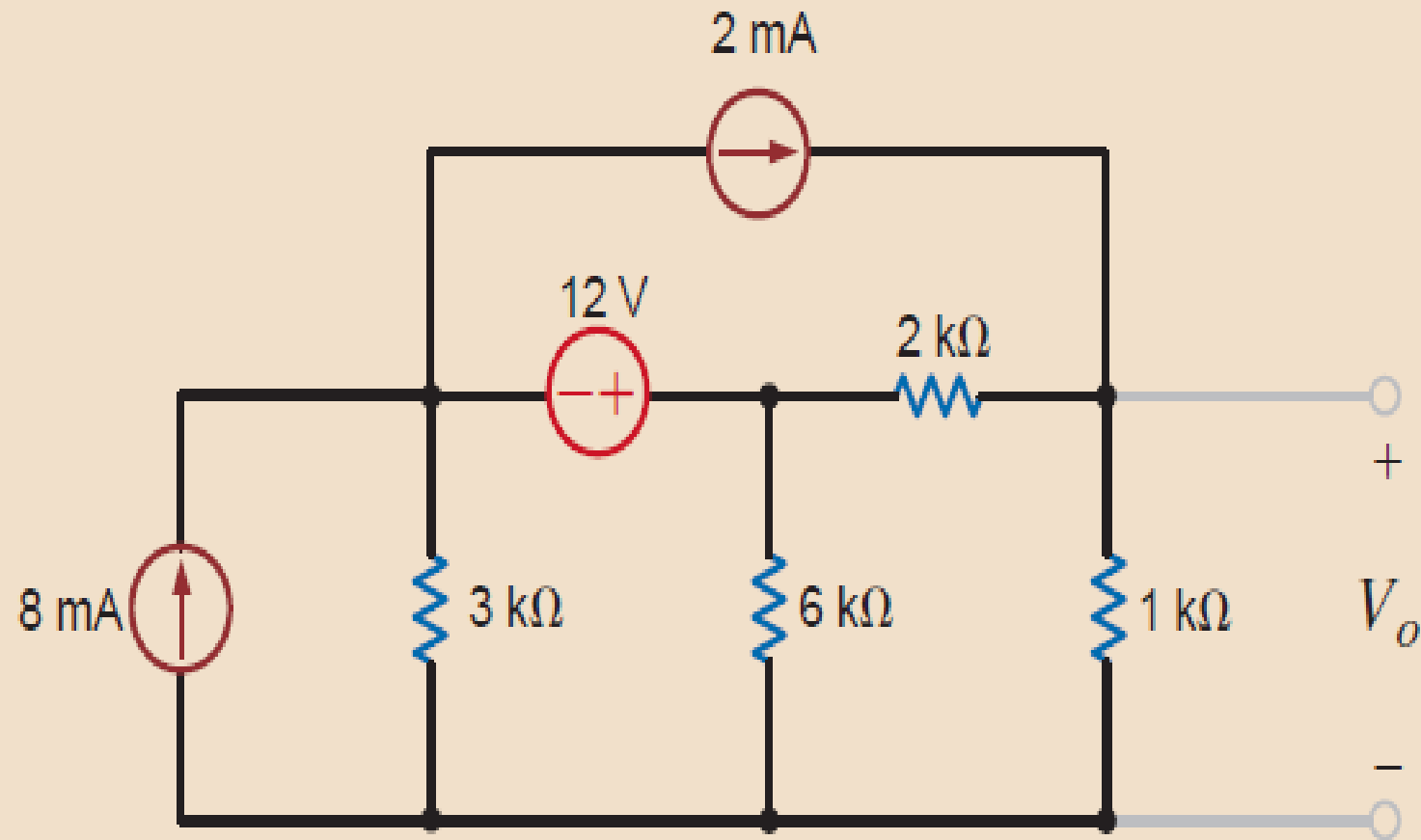


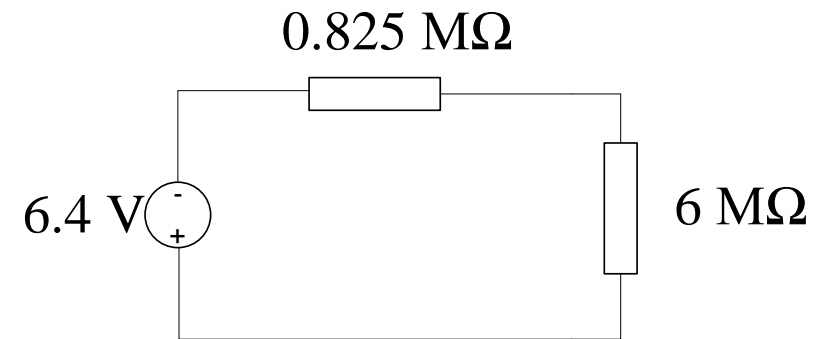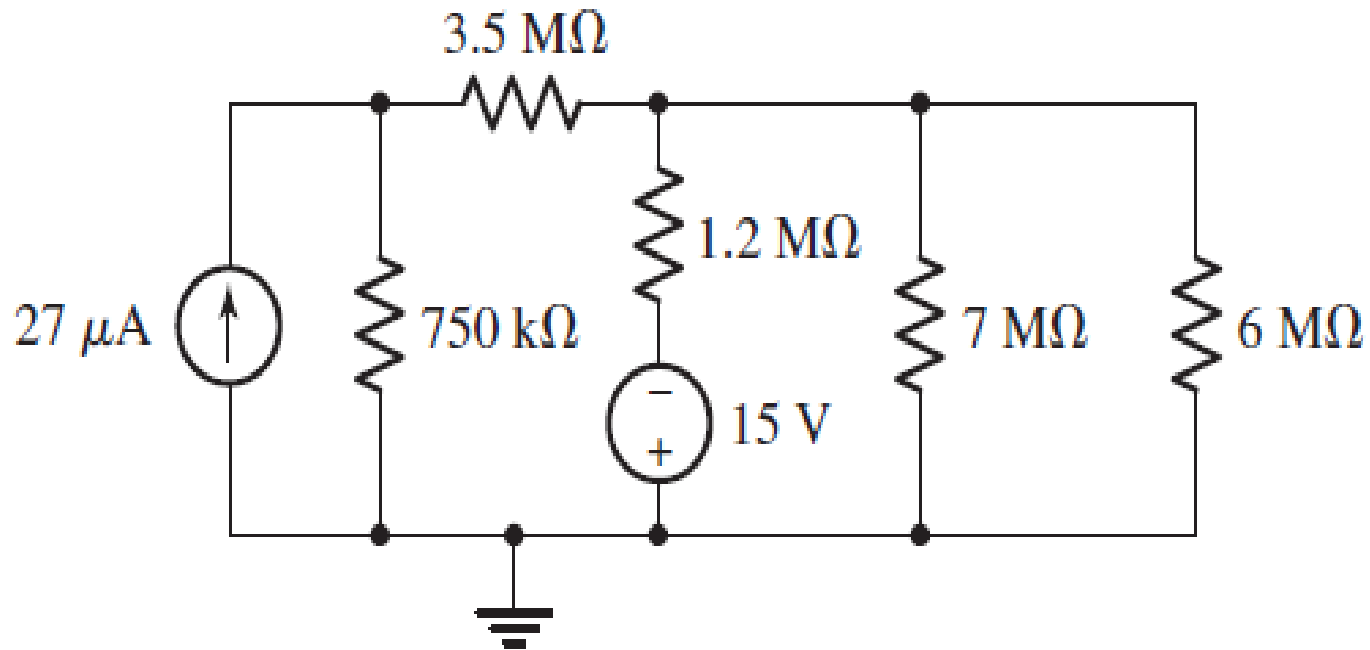(a) Using repeated source transformations, reduce the circuit below to a voltage source in series with a resistor, both of which are in series with the  $6\text{ M}\Omega$  resistor. (b) Calculate the power dissipated by the  $6\text{ M}\Omega$  resistor using your simplified circuit.




Power dissipated by the  $6\text{ M}\Omega$  is  $= 5.27\text{ }\mu\text{watt}$ .

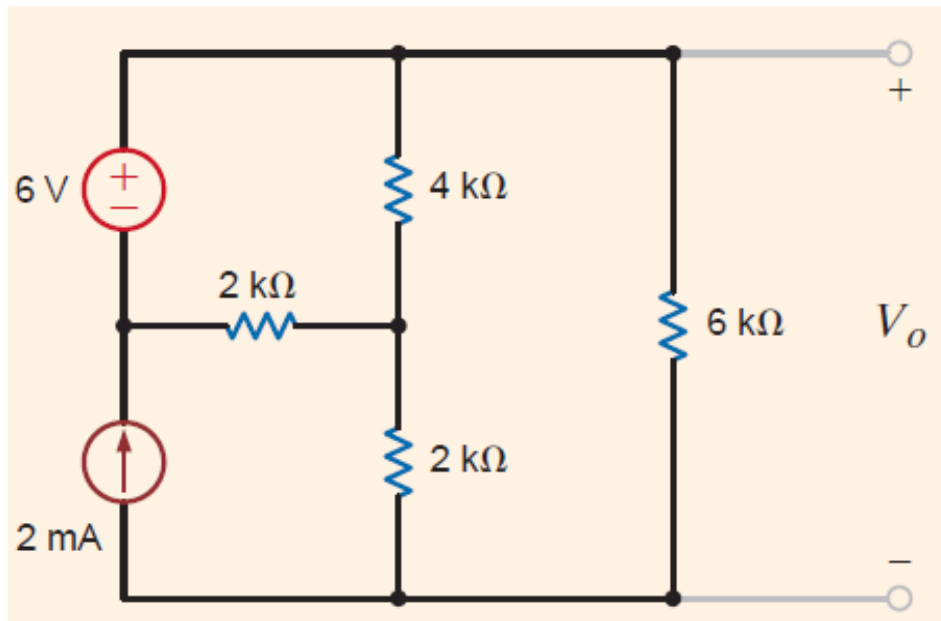
- Obtain the Thevenin and Norton equivalent circuits of the circuit shown below:




Thevenin's Equivalent

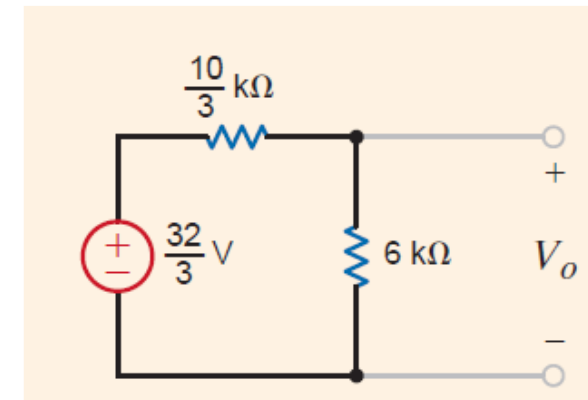

Norton's Equivalent

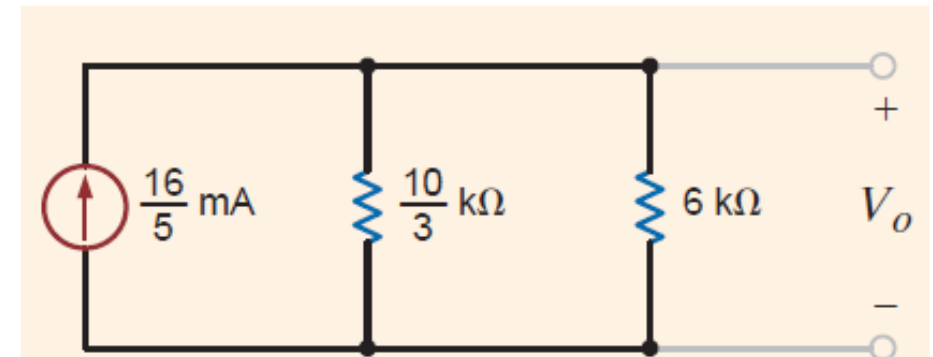


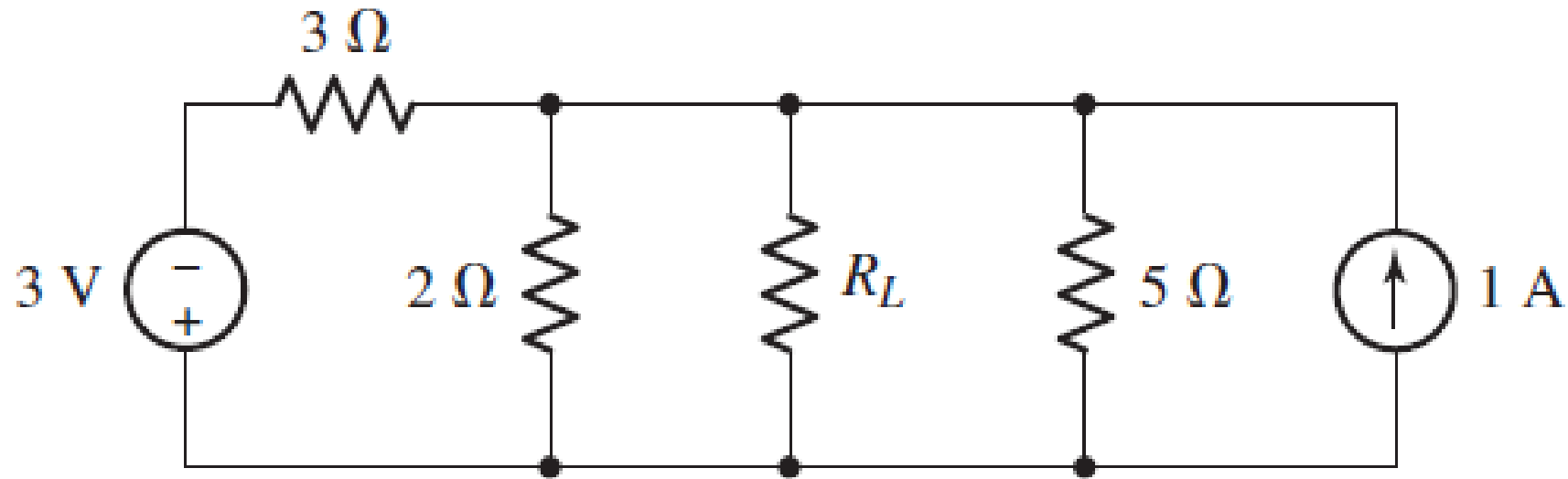- For the circuit given below, what value of  $R_L$  will ensure it absorbs the maximum possible amount of power?




$$R_{th} = 0.967 \, \Omega$$

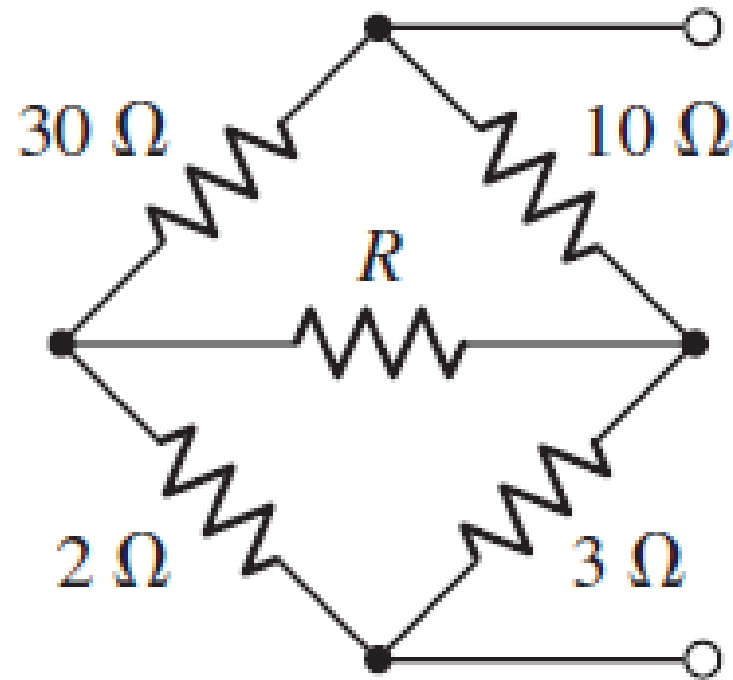- For the network of Fig. 5.97, select a value of  $R$  such that the network has an equivalent resistance of  $9\Omega$ . Round your answer to two significant figures



- Verify the reciprocity theorem:

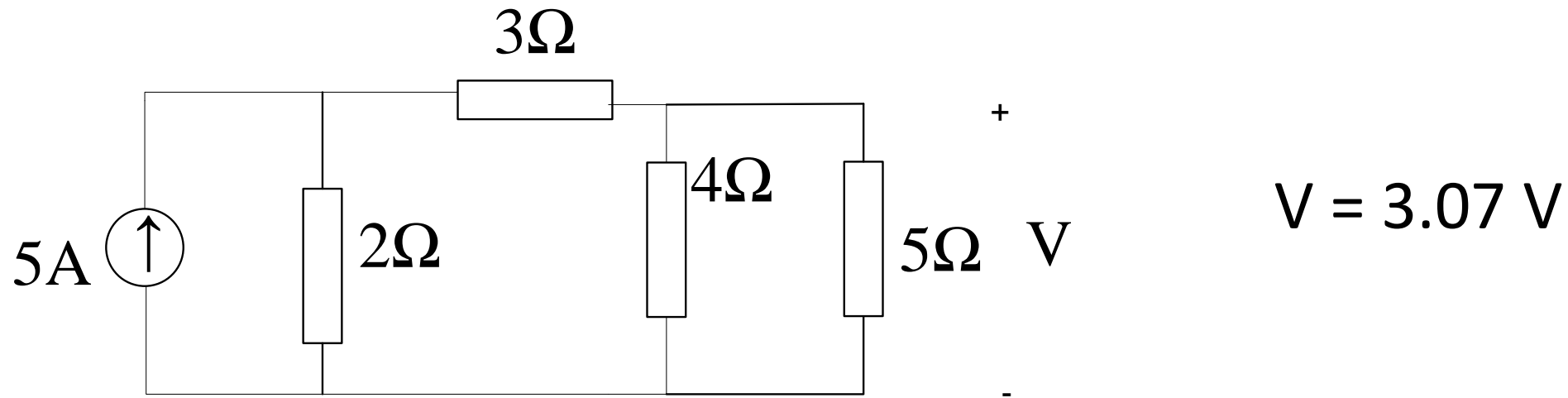

Note: To verify the reciprocity, interchange the source and observer, that is, place 5 A current source in parallel with 5 ohm resistor and calculate the voltage across the 2 ohm resistor. Then the voltage across 2 ohm resistor must be 3.07 V.