

## Indian Institute of Information Technology, Sri City, Chittoor

Name of the Exam: Basic Electronic Circuits Duration: 90 Mins. Max. Marks: 15

Roll No.: \_\_\_\_\_ Room No.: \_\_\_\_\_ Seat No.: \_\_\_\_\_

Invigilator's Signature: \_\_\_\_\_

	Q1	Q2	Q3	Q4	Q5	Total
Max. Marks	2	2	4	4	3	
Marks obtained						

## Instructions:

1. It's a closed book exam, no formula sheets, no text books, no hand written notes.
2. Mobile phones, and other smart gadgets are strictly not allowed, if anyone found with such items will be sent out of the examination hall and zero marks will be awarded.
3. Scientific calculator is allowed, but exchange of the same during the exam is strictly not allowed.
4. Answers written with pencil will not be evaluated.
5. You must write the answers in a clean and neat manner in the space provided.
6. No additional sheets will be provided.

Q1. (a) Determine the resistance of a circular bar of length 10 m and diameter  $\frac{4}{\sqrt{\pi}}$  m, which is made of a composite material having conductivity  $\sigma = 0.25$  milli S/m. (1 Mark)


$$R = \frac{l}{\sigma A}$$

$$l = 10 \text{ m}, D = \frac{4}{\sqrt{\pi}}, r = \frac{2}{\sqrt{\pi}}$$

$$A = \pi r^2 = 4 \quad \sigma = 0.25 \times 10^{-3}$$

$$R = \frac{10}{0.25 \times 10^{-3} \times 4} = 10 \text{ k}\Omega$$

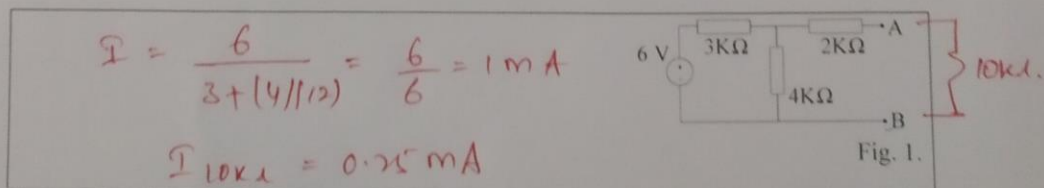(b) If this composite bar is connected across the terminals A and B as shown in Fig. 1, determine the current through the composite bar. (1 Mark)



$$I = \frac{6}{3 + (4 \parallel 10)} = \frac{6}{6} = 1 \text{ mA}$$

$$I_{10 \text{ k}\Omega} = 0.25 \text{ mA}$$

$$\frac{4 \times 10}{16} = 2.5$$

Q2. If the hybrid parameters of a two-port network shown in Fig. 2 are,  $h_{11} = 3 \Omega$ ;  $h_{12} = 2/3$ ;  $h_{21} = -2/3$ ; and  $h_{22} = 1/9 \text{ S}$ . Determine the values of  $R_1$ ,  $R_2$ , and  $R_3$ . (2 Marks)

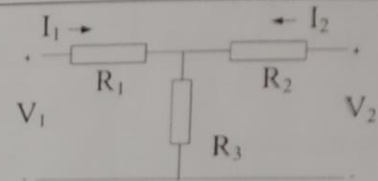


Fig. 2.

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 3 \quad \text{--- (1)}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = -\frac{R_3}{R_2 + R_3} = -\frac{2}{3} \quad \text{--- (2)}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_2}{R_2 + R_3} = 2/3 \quad \text{--- (3)}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_2 + R_3} = \frac{1}{9} \quad \text{--- (4)}$$

from (4)  $R_2 + R_3 = 9$  ; from (3)  $R_3 = \frac{2}{3} \times 9 = 6 \Omega$

$$R_2 = 3 \Omega \quad ; \quad R_1 = 1 \Omega$$

Rough work:

Q3. Determine the maximum power that can be delivered to the load resistance ' $R_L$ ' for the circuit shown in Fig. 3, note that, the transmission parameters of the two-port network are,  $A = 3/2$ ;  $B = 11/2 \Omega$ ;  $C = 1/2 \text{ S}$ ; and  $D = 5/2$ . (4 Marks)

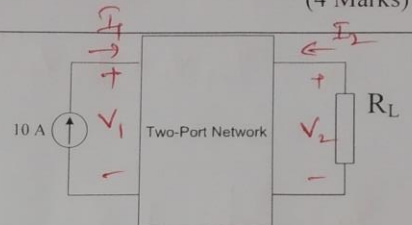


Fig. 3.

$$V_1 = \frac{3}{2} V_2 - \frac{11}{2} I_2 \rightarrow (1)$$

$$I_1 = \frac{1}{2} V_2 - \frac{5}{2} I_2 \rightarrow (2)$$

for  $V_2 = V_{OC}$ ;  $I_2 = 0$

$$\text{from (2)}$$


$$V_2 = 2 I_1 = 20 \text{ V} = V_{OC}$$

for  $V_2 = 0$ ;  $I_{sc} = -I_2$

$$I_1 = -\frac{5}{2} I_2 = \frac{5}{2} I_{sc}$$

$$I_{sc} = \frac{2}{5} I_1 = 4 \text{ A}$$
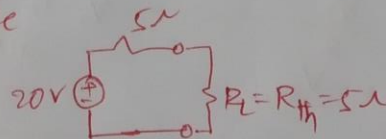
$$R_{th} = \frac{V_{OC}}{I_{sc}} = 5 \Omega$$





from Fig.

$$I_1 = 10 \text{ A}$$

$$I_2 = -\frac{V_2}{R_L}$$

open  $R_L$  to obtain

Theremin's equivalent

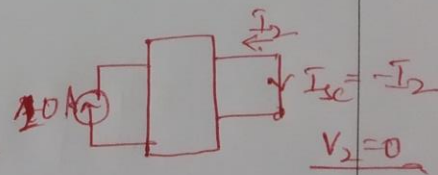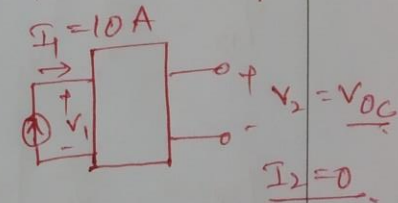

Rough Work:

$$P_{PL} = \frac{V_{OC}^2}{R_L} = \frac{100}{5} = 20 \text{ Watts}$$

(4 Marks)

Q4. Determine the Y-parameters of the network shown in Fig. 4.

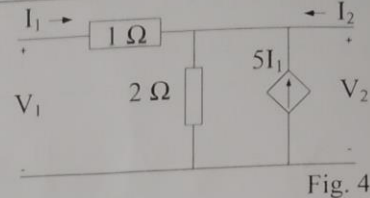


Fig. 4.

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 1 \text{ S}$$


$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-6 I_1}{V_1} = -6 \text{ S}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -1 \text{ S}$$


$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = 6.5 \text{ S}$$

$$6 I_1 + I_2 = \frac{V_2}{2}$$

using  $I_1 = -V_2$

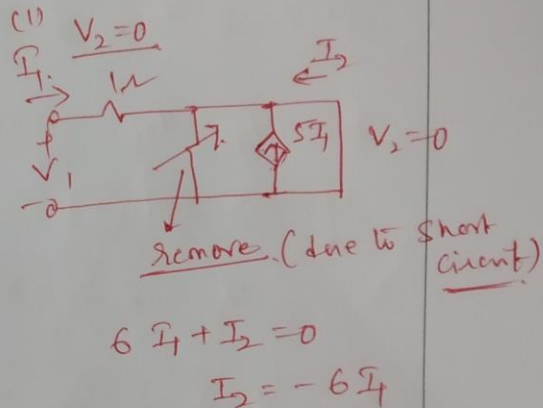

(ii)  $V_1=0$

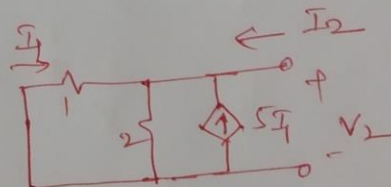

$V_2$  is the voltage drop across both 1 ohm & 2 ohm resistors

Rough Work:

$$-6 V_2 + I_2 = \frac{V_2}{2}$$

$$I_1 = -V_2$$

$$I_2 = 6.5 V_2 \Rightarrow \frac{I_2}{V_2} = 6.5$$

Obtain the Thevenin's equivalent of the circuit shown in Fig. 5.

(3 Marks)

(i)  $V_{OC} = V_x : I = 0$


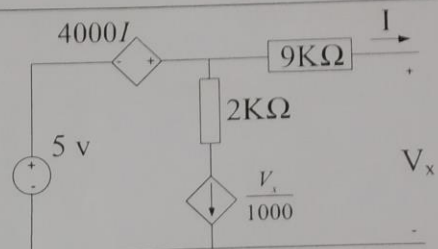
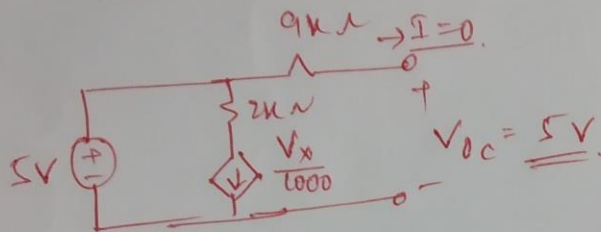



Fig. 5.

(ii)  $I = I_{SC} \quad V_d = 0$

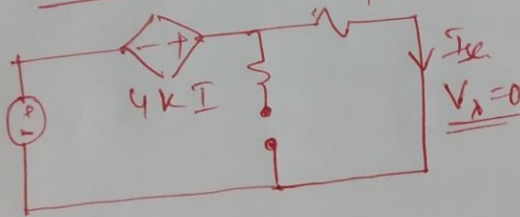

$$5 + 4k I_{SC} = 9k I_{SC}$$
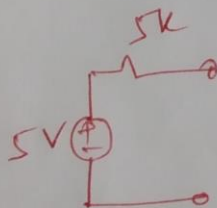
$$I_{SC} = \frac{5}{9k - 4k} = \frac{5}{5k} = 1mA$$



$$R_{TH} = \frac{5}{1mA} = 5k$$

Rough Work: